

Digital System Design with HDL (I)

Lecture 7

Dr. Ming Xu
Dept of Electrical & Electronic Engineering
XJTLU

1

In This Session

- Functions and Tasks
- Verilog for Combinational Circuits
 - Multiplexers
 - Decoders
 - Encoders
 - Comparators

2

Functions

- A function is a part of the code that may be re-used and thus separated from the other parts in a module.

- Syntax:

function [*size_or_type*] function_name;

input declarations

local variable declarations

procedural statements

endfunction

size_or_type (optional) is the returned type or range as [*msb:lsb*]. The default is a 1-bit value.

3


Functions

- Functions should have at least one input.
- The function name serves as the *only* output variable. No other output or inout is allowed.
- Functions are only defined within a module.

4

Functions

Example: a 16-to-1 multiplexer

 

```

module mux_f (W, S16, f);
  input [0:15] W;
  input [3:0] S16;
  output reg f;
  reg [0:3] M;

  function mux4to1;
    input [0:3] W;
    input [1:0] S;

    if (S == 0) mux4to1 = W[0];
    else if (S == 1) mux4to1 = W[1];
    else if (S == 2) mux4to1 = W[2];
    else if (S == 3) mux4to1 = W[3];
  endfunction

  always @(W, S16)
  begin
    M[0] = mux4to1(W[0:3], S16[1:0]);
    M[1] = mux4to1(W[4:7], S16[1:0]);
    M[2] = mux4to1(W[8:11], S16[1:0]);
    M[3] = mux4to1(W[12:15], S16[1:0]);
    f = mux4to1(M[0:3], S16[3:2]);
  end
endmodule

```

5

Tasks

- A task is a part of the code that may be re-used and thus separated from the other parts in a module.
- A task may have any number of inputs, outputs or inouts.
- A task does not return any value by its name.
- A task is like a subroutine.

6

Tasks

Syntax:

```


task task_name;
  input declarations
  output declarations
  local variable declarations
  procedural statements
endtask

```

7

Tasks

Example: a 16-to-1 multiplexer

 

```

module mux_t (W, S16, f);
  input [0:15] W;
  input [3:0] S16;
  output reg f;
  reg [0:3] M;


  task mux4to1;
    input [0:3] W;
    input [1:0] S;
    output Result;
    begin
      if (S == 0) Result = W[0];
      else if (S == 1) Result = W[1];
      else if (S == 2) Result = W[2];
      else if (S == 3) Result = W[3];
    end
  endtask

  always @(W, S16)
  begin
    mux4to1(W[0:3], S16[1:0], M[0]);
    mux4to1(W[4:7], S16[1:0], M[1]);
    mux4to1(W[8:11], S16[1:0], M[2]);
    mux4to1(W[12:15], S16[1:0], M[3]);
    mux4to1(M[0:3], S16[3:2], f);
  end
endmodule

```

8

Combinational circuits

 


- Outputs only depend on inputs
- Could include: gates, multiplexers, encoders, decoders, code converters, comparators ...
- Verilog description: gates, logic expression, behaviour

9

Multiplexers

Using conditional operators

 

```

module mux2to1 (w0, w1, s, f);
  input w0, w1, s;
  output f;

  assign f = s ? w1 : w0;

endmodule
    
```

Conditional operator
in continuous assignment

```

module mux2to1 (w0, w1, s, f);
  input w0, w1, s;
  output f;
  reg f;

  always @(w0 or w1 or s)
    f = s ? w1 : w0;


endmodule
    
```

Conditional operator
in procedural statement

10

Multiplexers

Using nesting conditional operators

 

```

module mux4to1 (w0, w1, w2, w3, S, f);
  input w0, w1, w2, w3;
  input [1:0] S;
  output f;

  assign f = S[1] ? (S[0] ? w3 : w2) : (S[0] ? w1 : w0);

endmodule
    
```

11

Multiplexers

Using If-else statements

```

module mux2to1 (w0, w1, s, f);
  input w0, w1, s;
  output f;
  reg f;

  always @(w0 or w1 or s)
    if (s == 0)
      f = w0;
    else
      f = w1;

endmodule
    
```

Using case statements

```


module mux4to1 (W, S, f);
  input [0:3] W;
  input [1:0] S;
  output f;
  reg f;

  always @(W or S)
    case (S)
      0: f = W[0];
      1: f = W[1];
      2: f = W[2];
      3: f = W[3];
    endcase

endmodule
    
```

12

Multiplexers

 

Hierarchical 16-to-1 Multiplexer

```

module mux16to1 (W, S16, f);
  input [0:15] W;
  input [3:0] S16;
  output f;
  wire [0:3] M;

  mux4to1 Mux1 (W[0:3], S16[1:0], M[0]);
  mux4to1 Mux2 (W[4:7], S16[1:0], M[1]);
  mux4to1 Mux3 (W[8:11], S16[1:0], M[2]);
  mux4to1 Mux4 (W[12:15], S16[1:0], M[3]);
  mux4to1 Mux5 (M[0:3], S16[3:2], f);

endmodule
  
```

13

Decoders

Decoder using case

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

Concatenate operator

Default for $En=0$

```

module dec2to4 (W, Y, En);
  input [1:0] W;
  input En;
  output [0:3] Y;
  reg [0:3] Y;

  always @(W or En)
    case ({En, W})
      3'b100: Y = 4'b1000;
      3'b101: Y = 4'b0100;
      3'b110: Y = 4'b0010;
      3'b111: Y = 4'b0001;
      default: Y = 4'b0000;
    endcase

endmodule
  
```

14

Decoders

Decoder using if-else, case

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

```

module dec2to4 (W, Y, En);
  input [1:0] W;
  input En;
  output [0:3] Y;
  reg [0:3] Y;

  always @(W or En)
    begin
      if (En == 0)
        Y = 4'b0000;
      else
        case (W)
          0: Y = 4'b1000;
          1: Y = 4'b0100;
          2: Y = 4'b0010;
          3: Y = 4'b0001;
        endcase
      end
    end

endmodule
  
```

15

Decoders

Decoder using for loops

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

```

module dec2to4 (W, Y, En);
  input [1:0] W;
  input En;
  output reg [0:3] Y;
  integer k;


  always @(W, En)
    for (k = 0; k <= 3; k = k+1)
      if ((W == k) && (En == 1))
        Y[k] = 1;
      else
        Y[k] = 0;

endmodule
  
```

16

Decoders


Hierarchical code for 4-16 decoder

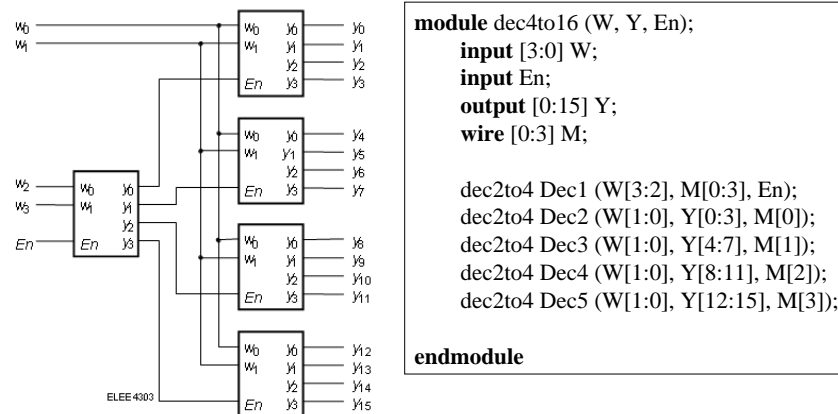

17

Decoders

BCD-to-7-segment decoder

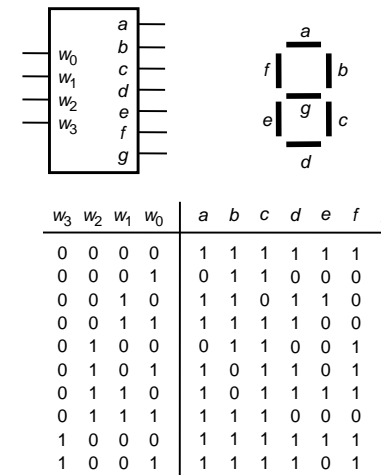


```

module seg7 (bcd, leds);
    input [3:0] bcd;
    output [1:7] leds;
    reg [1:7] leds;

    always @(bcd)
        case (bcd) //abcdefg
            0: leds = 7'b1111110;
            1: leds = 7'b0110000;
            2: leds = 7'b1101101;
            3: leds = 7'b1111001;
            4: leds = 7'b0110011;
            5: leds = 7'b1011011;
            6: leds = 7'b1011111;
            7: leds = 7'b1110000;
            8: leds = 7'b1111111;
            9: leds = 7'b1111011;
            default: leds = 7'bx;
        endcase
    endmodule
    
```

18

Encoders

 

```

module encoder (Code, Data);
    output [2:0] Code;
    input [7:0] Data;
    reg [2:0] Code;

    always@ ( Data )
        case (Data)
            8'b00000001 : Code = 3'b000;
            8'b00000010 : Code = 3'b001;
            8'b00000100 : Code = 3'b010;
            8'b00001000 : Code = 3'b011;
            8'b00010000 : Code = 3'b100;
            8'b00100000 : Code = 3'b101;
            8'b01000000 : Code = 3'b110;
            8'b10000000 : Code = 3'b111;
            default Code = 3'bx;
        endcase
    endmodule
    
```

19

Encoders

Priority encoder using casex

w ₃	w ₂	w ₁	w ₀	y ₁	y ₀	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

```

module priority (W, Y, z);
    input [3:0] W;
    output [1:0] Y;
    output z;
    reg [1:0] Y;
    reg z;

    always @(W)
        begin
            z = 1;
            casex(W)
                4'b1xxx: Y = 3;
                4'b01xx: Y = 2;
                4'b001x: Y = 1;
                4'b0001: Y = 0;
                default: begin
                    z = 0;
                    Y = 2'bx;
                end
            endcase
        end
    endmodule
    
```

20

Encoders

Priority encoder using for loops

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

```

module priority (W, Y, z);
  input [3:0] W;
  output reg [1:0] Y;
  output reg z;
  integer k;


  always @(W)
  begin
    Y = 2'bxx;
    z = 0;
    for (k = 0; k < 4; k = k+1)
      if (W[k])
        begin
          Y = k;
          z = 1;
        end
      end
    end

endmodule

```

21

Comparators

 

```

module compare (A, B, AeqB, AgtB, AltB);
  input [3:0] A, B;
  output reg AeqB, AgtB, AltB;

  always @(A, B)
  begin
    AeqB = 0;
    AgtB = 0;
    AltB = 0;
    if (A == B)
      AeqB = 1;
    else if (A > B)
      AgtB = 1;
    else
      AltB = 1;
    end
endmodule

```

22