

Digital System Design with HDL (I)

Lecture 5

Dr. Ming Xu

Dept of Electrical & Electronic Engineering
XJTLU

1

In This Session

- Primitive Instantiations
- Continuous Assignments
- Procedural Statements
 - Procedural Assignment Statements

2

Primitive Instantiations

A circuit can be described using predefined modules.

```
gate_type [instance_name] (output_port, input_port {,  
input_port });
```

```
gate_type # (delay) [instance_name] (output_port,  
input_port {, input_port });
```

- *gate_type*: the type of gate
- *Instance_name*: optional.
- *delay*: propagation delay in time units.

3

Primitive Instantiations

Example: Structural specification of a full-adder

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  wire z1, z2, z3, z4;  
  
  and And1 (z1, x, y);  
  and And2 (z2, x, Cin);  
  and And3 (z3, y, Cin);  
  or Or1 (Cout, z1, z2, z3);  
  xor Xor1 (z4, x, y);  
  xor Xor2 (s, z4, Cin);  
  
endmodule
```

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  
  and (z1, x, y);  
  and (z2, x, Cin);  
  and (z3, y, Cin);  
  or (Cout, z1, z2, z3);  
  xor (z4, x, y);  
  xor (s, z4, Cin);  
  
endmodule
```

4

Primitive Instantiations

Gate Types

Name	Description	Usage
and	$f = (a \cdot b \dots)$	and (f, a, b, \dots)
nand	$f = \overline{(a \cdot b \dots)}$	nand (f, a, b, \dots)
or	$f = (a + b + \dots)$	or (f, a, b, \dots)
nor	$f = \overline{(a + b + \dots)}$	nor (f, a, b, \dots)
xor	$f = (a \oplus b \oplus \dots)$	xor (f, a, b, \dots)
xnor	$f = (a \odot b \odot \dots)$	xnor (f, a, b, \dots)
not	$f = \bar{a}$	not (f, a)

Primitive Instantiations

Gate Types

- notif** and **bufif** gates are tri-state buffers.

Name	Description	Usage
buf	$f = a$	buf (f, a)
notif0	$f = (!e ? \bar{a} : 'bz)$	notif0 (f, a, e)
notif1	$f = (e ? \bar{a} : 'bz)$	notif1 (f, a, e)
bufif0	$f = (!e ? a : 'bz)$	bufif0 (f, a, e)
bufif1	$f = (e ? a : 'bz)$	bufif1 (f, a, e)

6

Continuous Assignments

- Continuous assignments model combinational logic.
- Each time a signal on the right-hand side changes, the net on the left-hand side is re-evaluated.

Explicit Continuous Assignment

```
net_type [size] net_name;
assign net_name = expression;
```


Implicit Continuous Assignment

```
net_type [size] net_name = expression;
```

7

Continuous Assignments

Example

 

```
module example3 (x1, x2, x3, f);
  input x1, x2, x3;
  output f;

  assign f = (x1 & x2) | (~x2 & x3);

endmodule
```

8

Continuous Assignments

- Multiple assignments can be specified in one assign statement (separated by commas)
assign Cout = (x & y) | (x & Cin) | (y & Cin),
 s = x ^ y ^ z;
- Multiple assignments can be combined with a net (wire, tri) declaration.
wire s = x ^ y,
 c = x & y;
- Continuous assignments are **concurrent** statements; their ordering in the code does not matter.

9

Procedural Statements

- Procedural statements are evaluated in the order in which they appear.
- Procedural statements must be contained in **always** (or **initial**) blocks, or **function** or **task** blocks that are called only from inside **always** (or **initial**) blocks.
- **always** procedural blocks process statements *repeatedly*.
- **initial** procedural blocks process statements *one time*.

10

always Block

always @(sensitivity_list)

[begin]

 [procedural assignment statements]

 [programming constructs]

[end]

- If the value of a signal in the *sensitive list* changes, all the statements are evaluated sequentially.
- The signals are separated by keyword **or** or comma in Verilog 2001.

11


always Block

- Level-sensitive **always** block
 - **always** @ (signal1 **or** signal2)
 - Used for combinational circuits and latches
- Edge-sensitive **always** block
 - **always** @ (**posedge** clk)
 - Response to positive edge of clk signal
 - **always** @ (**negedge** clk)
 - Response to negative edge of clk signal
 - Used for sequential circuits and flip-flops

12

always Block

Example:
a combinational logic circuit

 

```

module example5 (x1, x2, x3, f);
  input x1, x2, x3;
  output f;
  reg f;

  always @(x1 or x2 or x3)
    if (x2 == 1)
      f = x1;
    else
      f = x3;


endmodule

```

13

always Block

Example: D-type flip-flop

 

```

module flipflop (D, Clock, Q);
  input D, Clock;
  output Q;
  reg Q;

  always @(posedge Clock)
    Q = D;

endmodule

```

14

Procedural Assignment Statements

- **=**
Blocking assignments – evaluate *in order*
 begin
 Q1 = D;
 Q2 = Q1; // new Q1 goes to Q2.
 end
- **<=**
No-blocking assignments – evaluate *in parallel*
 begin
 Q1<= D;
 Q2<= Q1; // old Q1 goes to Q2
 end
 The order of statements doesn't matter

15


Procedural Assignment Statements

- For *blocking assignments*, the values of variables in each statement are the new values set by any preceding statements in the **always** block.
- For *non-blocking assignments*, the values of variables are the values at the beginning of the **always** block.
- Although the statements inside each **always** block are evaluated in order, each entire **always** block is still like a concurrent statement.

16

Procedural Assignment Statements

Blocking and non-blocking assignments

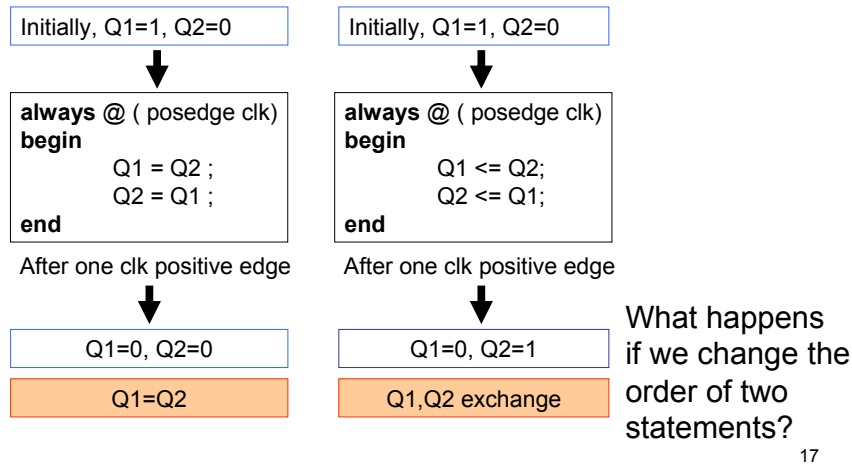


Procedural Assignment Statements

Example: Blocking assignments

```
module example7_3 (D, Clock, Q1, Q2);
    input D, Clock;
    output Q1, Q2;
    reg Q1, Q2;

    always @(posedge Clock)
    begin
        Q1 = D;
        Q2 = Q1;
    end

endmodule
```

 


Procedural Assignment Statements

Example: No-blocking assignments

```
module example7_4 (D, Clock, Q1, Q2);
    input D, Clock;
    output Q1, Q2;
    reg Q1, Q2;

    always @(posedge Clock)
    begin
        Q1 <= D;
        Q2 <= Q1;
    end

endmodule
```

 

Procedural Assignment Statements

Recommendations

- It is better to use **blocking** assignments when describing **combinational** circuits
- It is better to using **no-blocking** assignments to describe **sequential** circuits