

# Digital System Design with HDL (I)

## Lecture 11

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU


1

## In This Session

- Moore-Type FSMs
- Mealy-Type FSMs
- Verilog Code for FSMs

2


## General Form of A Sequential Circuit.

 

- Sequential circuits are called **finite state machines (FSM)**.
- Combinational circuit 1 has inputs from the input W and the state Q of the flip-flops.
- The output Z always depends on the state Q of the flip-flops. It may also depend on the input W.

3

## General Form of A Sequential Circuit.

 

- The sequential circuits whose outputs depend only on the state of the circuit are of **Moore type**.
- Those whose outputs depend on both the state and the inputs are of **Mealy type**.

4

## Moore State Model.

We wish to design such a circuit:

- The circuit has one input  $w$  and one output  $z$ .
- All changes in the circuit occur on the positive edge of a clock signal.
- The output  $z$  is 1 if during the past two clock cycles  $w$  was 1. Otherwise  $z$  is 0.

Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0


Sequences of input and output signals.

5
 
## Moore State Model.

State Diagram

- State A:  $w$  is 0 during past 1 clock cycle.
- State B:  $w$  has been 1 for just 1 clock cycle.
- State C:  $w$  has been 1 for 2 clock cycles.



6

## Moore State Model.

State Table


Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

	Present state $y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

7

## Moore State Model.

Next-State and Output Expressions

 


8

## Moore State Model.

Implementation

Output  $z$  depends on the state only.

 

9

## Moore State Model.


Alternative State Assignment

	Present state $y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	$dd$	$dd$	$d$

10

## Moore State Model.

Improved Implementation

 

11

## Mealy State Model.

We wish to design such a circuit:

- The circuit has one input  $w$  and one output  $z$ .
- The output  $z$  is 1 in the clock cycle when the second occurrence of  $w = 1$  is detected. Otherwise  $z$  is 0.

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	1	0	0	1	1	0	0


Sequences of input and output signals.

12

## Mealy State Model.
 
### State Diagram

- State A:  $w$  is 0, producing an output  $z = 0$ .
- State B:  $w$  is 1.
- If  $w = 1$  for two consecutive clock cycles, the machine remains in state B and produce an output  $z = 1$ .



13

## Mealy State Model.

### State Table

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
$y$	$Y$	$Y$	$z$	$z$
A	0	0	0	0
B	1	0	0	1


14

## Mealy State Model.

### Implementation

$$Y = D = w$$

$$z = wy$$

 

Output  $z$  depends on both the state and the input.

15

## Verilog Code for the Moore FSM.

```

module simple (Clock, Resetn, w, z);
  input Clock, Resetn, w;
  output z;
  reg [2:1] y, Y;
  parameter [2:1] A = 2'b00, B = 2'b01, C = 2'b10;

```

```


  // Define the next state combinational circuit

```

```

  always @(w, y)
    case (y)
      A: if (w) Y = B;
         else Y = A;
      B: if (w) Y = C;
         else Y = A;
      C: if (w) Y = C;
         else Y = A;
      default: Y = 2'bxx;
    endcase

```

 

```

  // Define the sequential block
  always @(negedge Resetn, posedge Clock)
    if (Resetn == 0) y <= A;
    else y <= Y;

```

```

  // Define output
  assign z = (y == C);


```

```

endmodule

```

## Verilog Code for the Moore FSM.

 

```

module simple (Clock, Resetn, w, z);
  input Clock, Resetn, w;
  output z;
  reg [2:1] y;
  parameter [2:1] A = 2'b00, B = 2'b01, C = 2'b10;

  // Define the sequential block
  always @(negedge Resetn, posedge Clock)
    if (Resetn == 0) y <= A;
    else
      case (y)
        A: if (w) y <= B;
            else y <= A;
        B: if (w) y <= C;
            else y <= A;
        C: if (w) y <= C;
            else y <= A;
        default: y <= 2'bxx;
      endcase
  end

  // Define output
  assign z = (y == C);
endmodule
  
```


17

## Verilog Code for the Mealy FSM.

```

module mealy (Clock, Resetn, w, z);
  input Clock, Resetn, w;
  output reg z;
  reg y, Y;
  parameter A = 1'b0, B = 1'b1;

   always @(w, y)
    case (y)
      A: if (w)
          begin
            z = 0;
            Y = B;
          end
        else
          begin
            z = 0;
            Y = A;
          end
    endcase
  end
  
```



```

    B: if (w)
        begin
          z = 1;
          Y = B;
        end
      else
        begin
          z = 0;
          Y = A;
        end
    endcase

  // Define the sequential block
  always @(negedge Resetn, posedge Clock)
    if (Resetn == 0) y <= A;
    else y <= Y;
  end
endmodule
  
```

18


## Verilog Code for the FSM.

### State Assignment

- State assignments are specified by a **parameter** statement in Verilog code.
- Verilog compilers can recognize the code for an FSM.
- They can optimize the implementation by looking for a better state assignment based on the cost of implementation.
- The user can either allow the compiler to optimize the state assignment or suppress it.

19

## Verilog Code for the FSM.

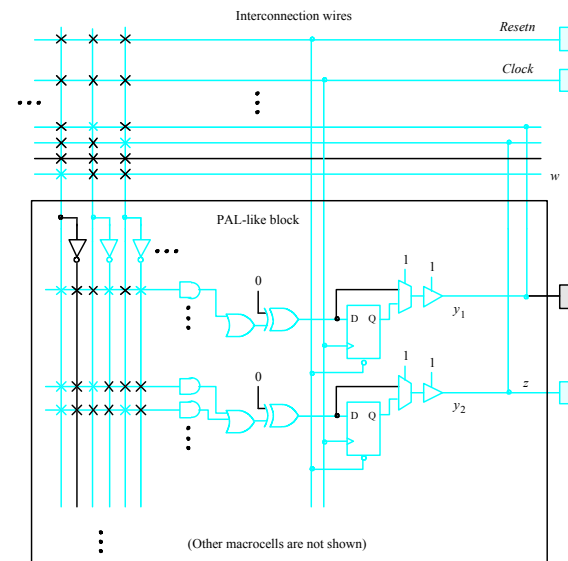

- The code for the Moore one is synthesised in a CPLD.
- The used parts are highlighted in blue.

$$Y_1 = w y_1 \bar{y}_2$$

$$Y_2 = w y_1 + w y_2$$

$$= w (y_1 + y_2)$$

$$z = y_2$$

20