

Digital System Design with HDL (I)

Lecture 13

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

1

In This Session

- Design Example — Bus Structure


2

The Functions

- A digital system contains a set of registers used to store data.
- Each register is connected to a bus, which is used to transfer data into and out of the register.
- Data can be also placed on the bus from an external circuit block.
- At any time only one register or the external block can put data onto the bus.


3

Bus Structure for Digital Systems

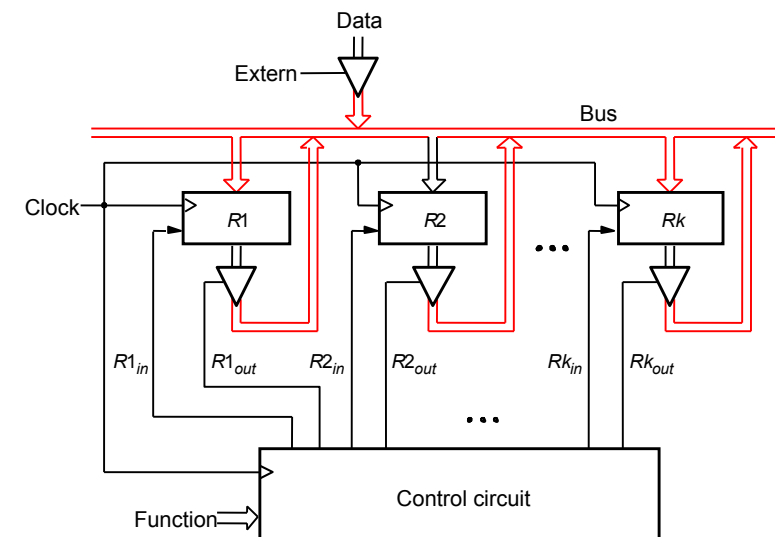

4


Connecting Registers to a Bus

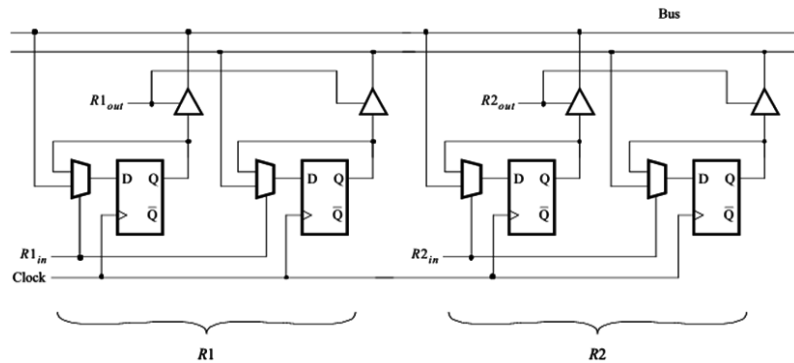

2-bit bus connecting: 2 registers


5

Swapping operation

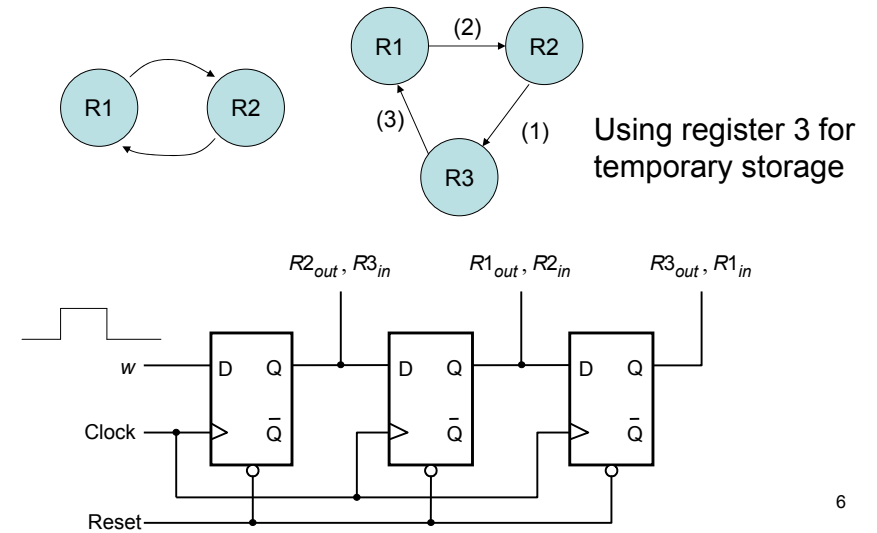

6

Verilog for Swapping

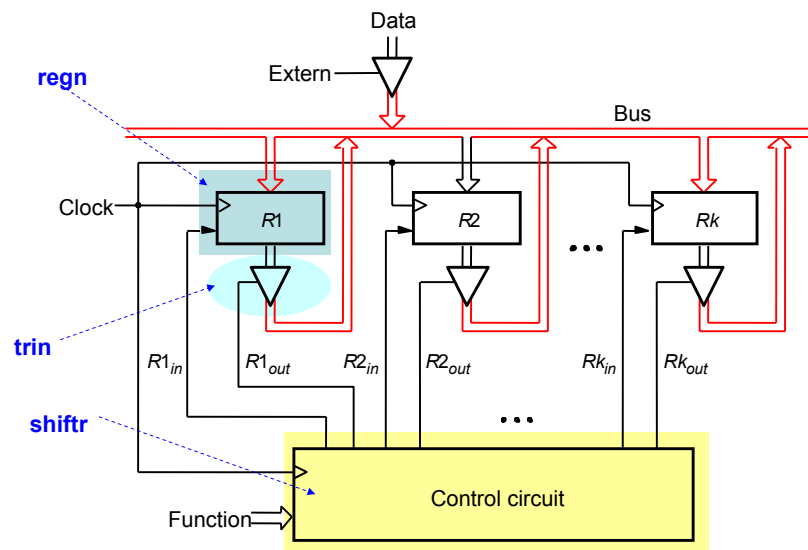

7


N-bit Register Module

```

module regn (R, Rin, Clock, Q);
  parameter n = 8;
  input [n-1:0] R;
  input Rin, Clock;
  output [n-1:0] Q;
  reg [n-1:0] Q;

  always @(posedge Clock)
    if (Rin)
      Q <= R;

endmodule
    
```

 

8

Tri-State Module


```

module trin (Y, E, F);
  parameter n = 8;
  input [n-1:0] Y;
  input E;
  output [n-1:0] F;
  wire [n-1:0] F;

  assign F = E ? Y : 'bz;

endmodule

```

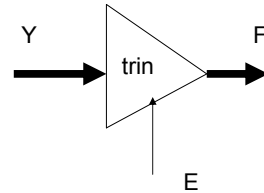

9


Control Circuit Module

```

module shift (Resetn, w, Clock, Q);
  parameter m = 4;
  input Resetn, w, Clock;
  output [1:m] Q;
  reg [1:m] Q;
  integer k;


  always @(negedge Resetn or posedge Clock)
    if (!Resetn)
      Q <= 0;
    else
      begin
        for (k = m; k > 1; k = k-1)
          Q[k] <= Q[k-1];
        Q[1] <= w;
      end
    endmodule

```

 

10

A Digital System for Swap

 

```

module swap (Data, Resetn, w, Clock,
  Extern, RinExt, BusWires);

  input [7:0] Data;
  input Resetn, w, Clock, Extern;
  input [1:3] RinExt;
  output [7:0] BusWires;
  tri [7:0] BusWires;
  wire [1:3] Rin, Rout, Q;
  wire [7:0] R1, R2, R3;

  shift control (Resetn, w, Clock, Q);
  defparam control.m = 3;

```

Q[1]: $R2_{out}, R3_{in}$
 Q[2]: $R1_{out}, R2_{in}$
 Q[3]: $R3_{out}, R1_{in}$

RinExt [i] allows external data to be loaded into Ri

```

assign Rin[1] = RinExt[1] | Q[3];
assign Rin[2] = RinExt[2] | Q[2];
assign Rin[3] = RinExt[3] | Q[1];
assign Rout[1] = Q[2];
assign Rout[2] = Q[1];
assign Rout[3] = Q[3];

  regn reg_1 (BusWires, Rin[1], Clock, R1);
  regn reg_2 (BusWires, Rin[2], Clock, R2);
  regn reg_3 (BusWires, Rin[3], Clock, R3);


  trin tri_ext (Data, Extern, BusWires);
  trin tri_1 (R1, Rout[1], BusWires);
  trin tri_2 (R2, Rout[2], BusWires);
  trin tri_3 (R3, Rout[3], BusWires);

```

endmodule


11

Swap Based on Multiplexers

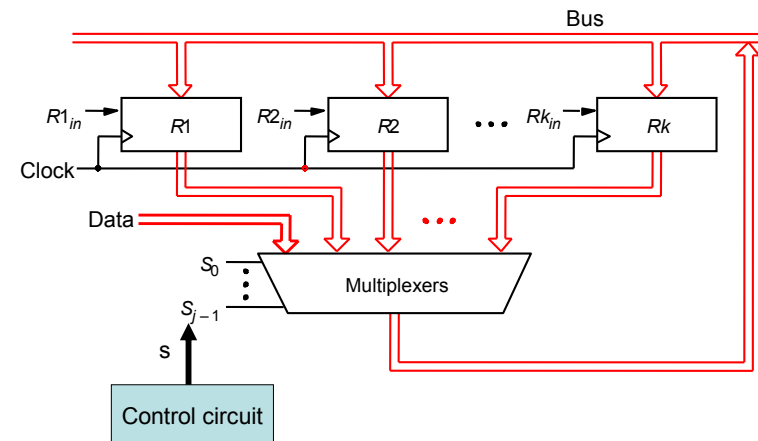

12

Swap using multiplexers

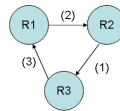

```

module swapmux (Data, Resetn, w, Clock,
RinExt, BusWires);
  input [7:0] Data;
  input Resetn, w, Clock;
  input [1:3] RinExt;
  output [7:0] BusWires;
  reg [7:0] BusWires;
  wire [1:3] Rin, Q;
  wire [7:0] R1, R2, R3;

  shiftr control (Resetn, w, Clock, Q);
  defparam control.m = 3;

  assign Rin[1] = RinExt[1] | Q[3];
  assign Rin[2] = RinExt[2] | Q[2];
  assign Rin[3] = RinExt[3] | Q[1];
    
```

```

  regn reg_1 (BusWires, Rin[1], Clock, R1);
  regn reg_2 (BusWires, Rin[2], Clock, R2);
  regn reg_3 (BusWires, Rin[3], Clock, R3);

  always @(Q or Data or R1 or R2 or R3)
  begin
    if (Q == 3'b000) BusWires = Data;
    else if (Q == 3'b100) BusWires = R2;
    else if (Q == 3'b010) BusWires = R1;
    else BusWires = R3;
  end

endmodule
    
```


Q[1]: R2_{out}, R3_{in}
Q[2]: R1_{out}, R2_{in}
Q[3]: R3_{out}, R1_{in}

Q [1:3]: Q[1], Q[2], Q[3]

Q[1]: R2_{out}
Q[2]: R1_{out}
Q[3]: R3_{out}

13

Simulation


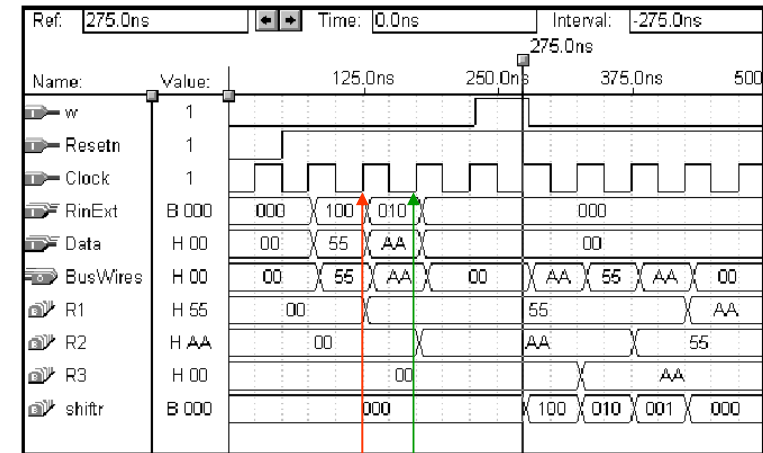


w, RinExt, Data are generated elsewhere but aligned with Clock.

AA written into R2
55 written into R1

14

Simulation

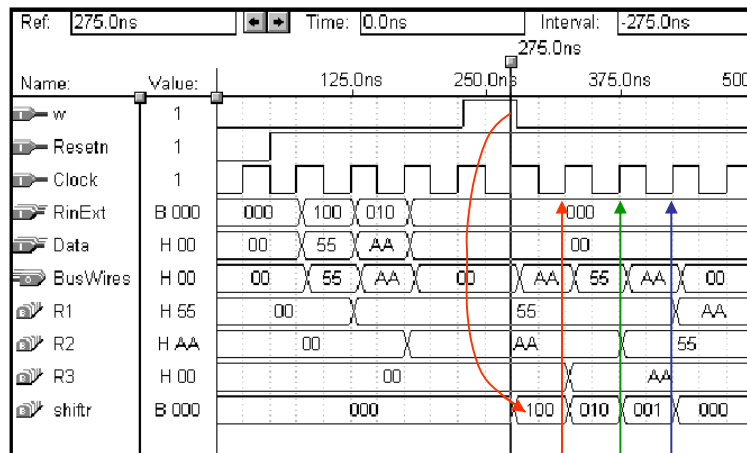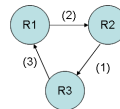

R3 => R1
R1 => R2
R2 => R3

15